

Analog Circuits

Day-9

Power Amplifiers

Contents:


- Classification of Amplifier
- Class A Power amplifier and its Analysis
 - ♣ Example
- Harmonic Distortions
- Class B push-pull amplifiers and its Analysis
 - ♣ Example
- Complementary Symmetry push-pull Amplifier
- Class AB Power Amplifier
- Class C Power Amplifier
- Thermal Stability and Heat sinks
- Distortion in Amplifiers

Introduction

- Power amplifiers are used to deliver a relatively **high amount of power**, usually **to a low resistance load**.
- Typical load values range from 300W (for transmission antennas) to 8W (for audio speaker).
- Although these load values do not cover every possibility, they do illustrate the fact that power amplifiers **usually drive low-resistance loads**.
- Typical output power rating of a power amplifier will be **1W or higher**.
- **Ideal** power amplifier will deliver **100%** of the power it draws from the supply to load. In **practice**, this can never occur.
- The reason for this is the fact that the components in the amplifier will all **dissipate** some of the power that is being drawn from the supply.

Concept of Power Amplifier

- Provide *sufficient power* to an output load to drive other power device.
- To deliver a large current to a small load resistance e.g. audio speaker;
- To deliver a large voltage to a large load resistance e.g. switching power supply;
- To provide a low output resistance in order to avoid loss of gain and to maintain linearity (to minimize harmonic distortion)
- To deliver power to the *load efficiently*

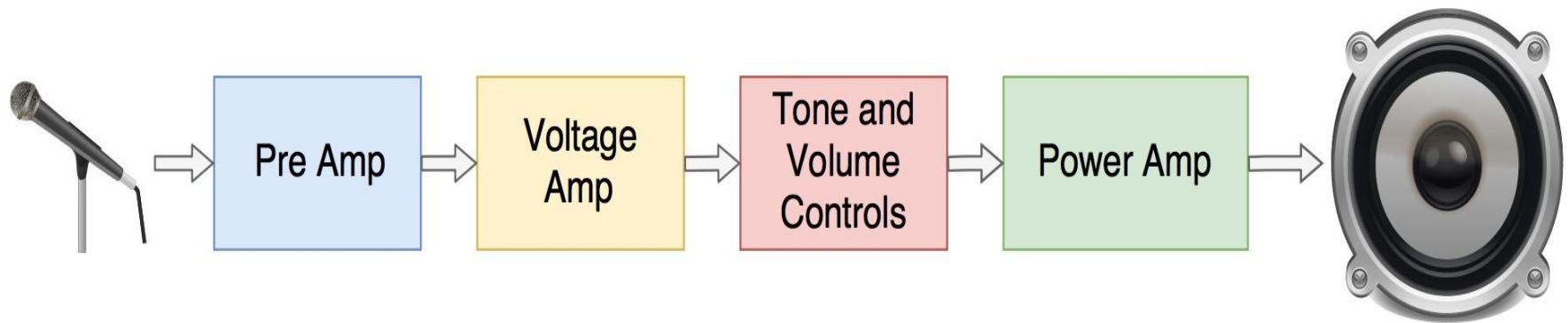

INPUT

Block Diagram of an Audio Amplifier

OUTPUT


ELECTRONICS HU3

Power Amplifier Power Dissipation

The **total** amount of power being dissipated by the amplifier, P_{tot} , is

$$P_{tot} = P_1 + P_2 + P_C + P_T + P_E$$

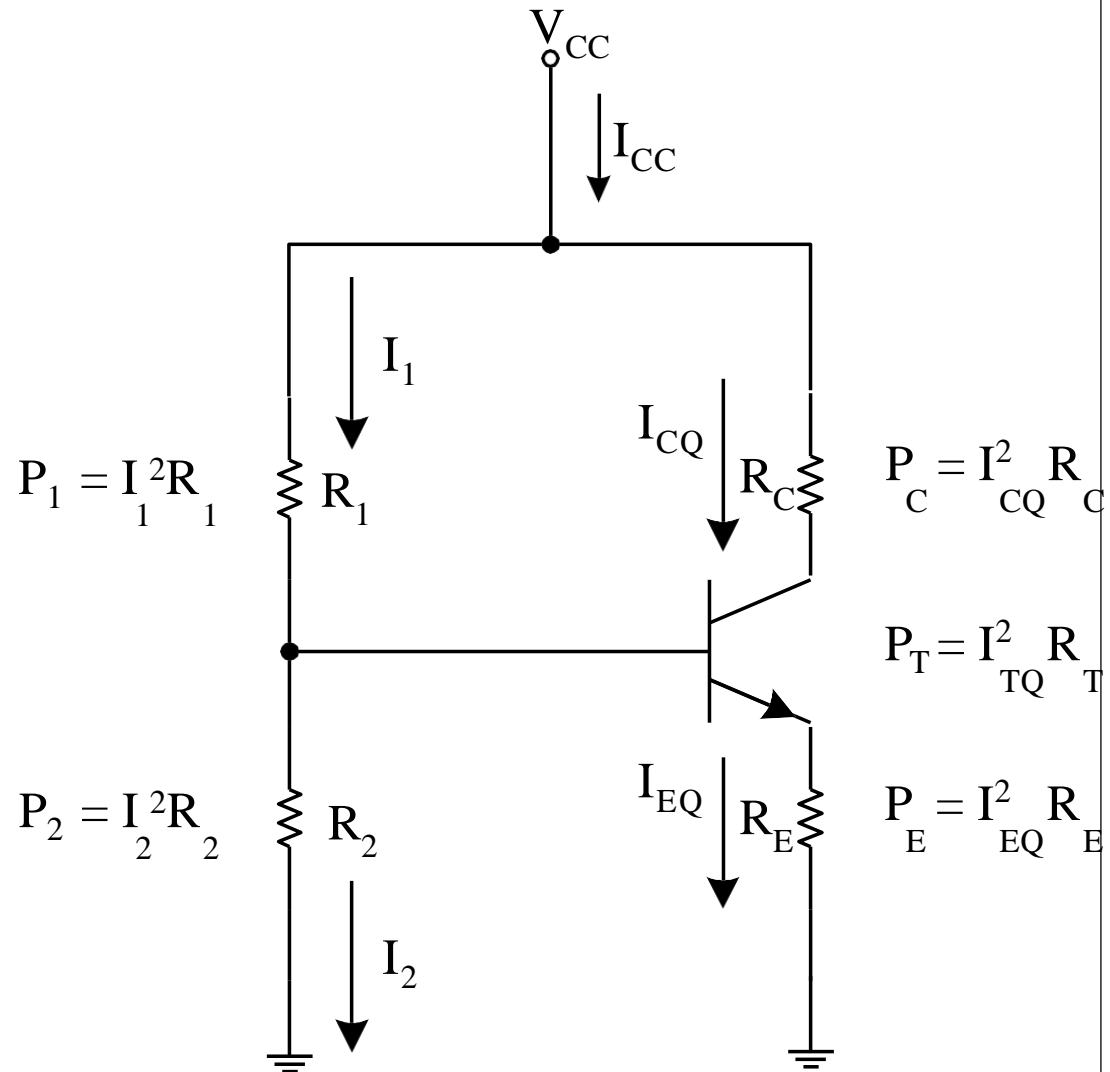The difference between this total value and the total power being drawn from the supply is the power that actually goes to the **load** – **i.e. output power**.



Power Amplifier Efficiency η

- A **figure of merit** for the power amplifier is its efficiency, η .
- **Efficiency (η)** of an amplifier is defined as the ratio of ac output power (power delivered to load) to dc input power .
- B y formula:
$$\eta = \frac{\text{ac output power}}{\text{dc input power}} \times 100\% = \frac{P_o(ac)}{P_i(dc)} \times 100\%$$
- A s we will see, certain amplifier configurations have much higher efficiency ratings than others.
- This is primary consideration when deciding which type of power amplifier to use for a specific application.


Power Amplifiers Classification

(Depending on Type of output load)


- ☐ **AUDIO AMPLIFIERS**
- ☐ **RADIO FREQUENCY AMPLIFIERS**
- ☐ **D C POWER AMPLIFIERS**

Power Amplifiers Classification


Class-A Power Amplifier:

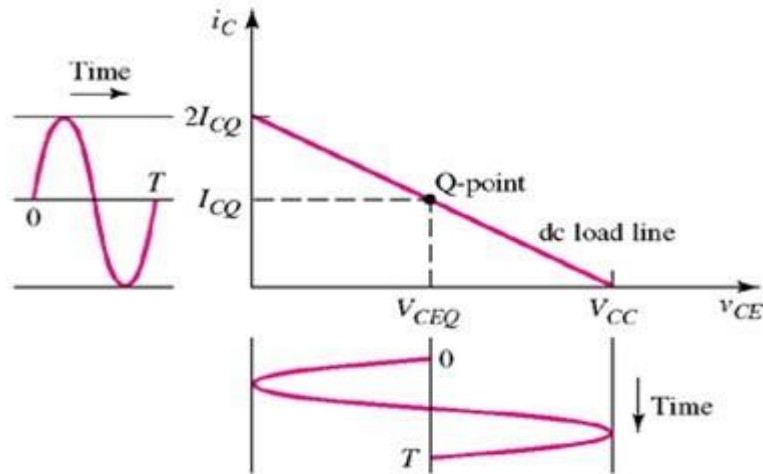


Class-B Power Amplifier:

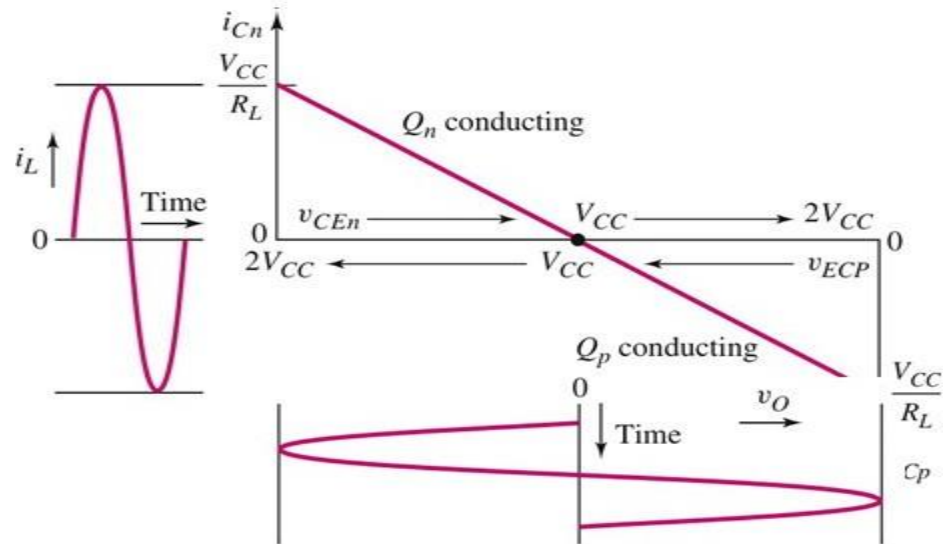


Class-C Power Amplifier:

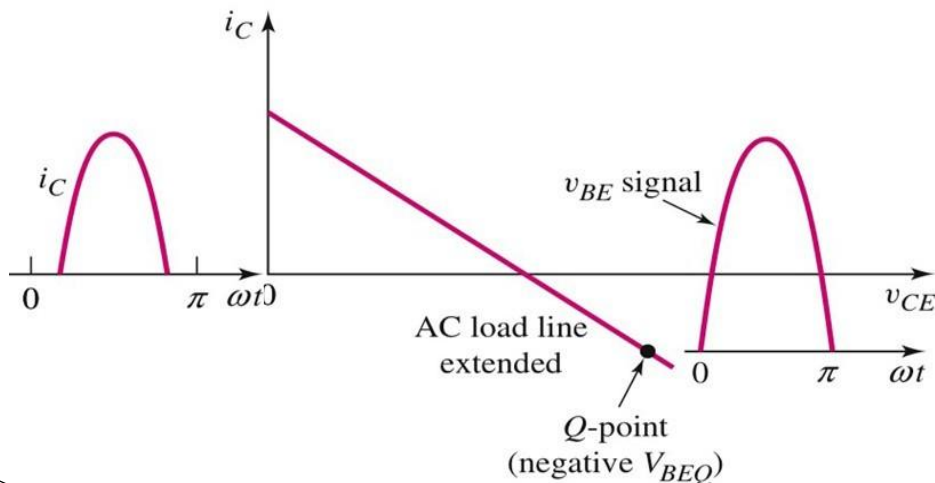

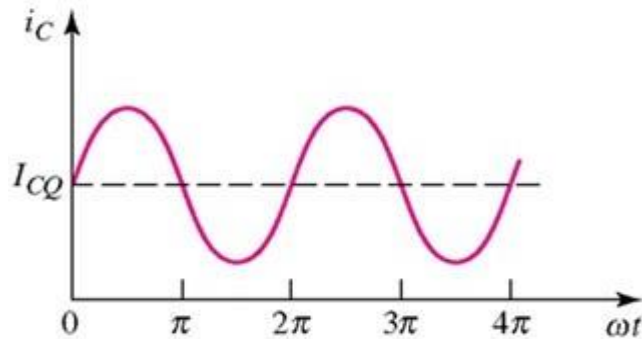
Class A - The transistor conducts during the whole cycle of sinusoidal input signal



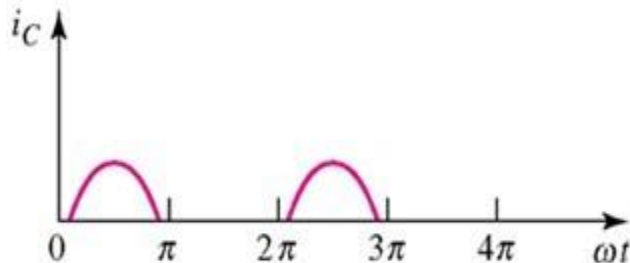
Class C - The transistor conducts for less than half a cycle of input signal



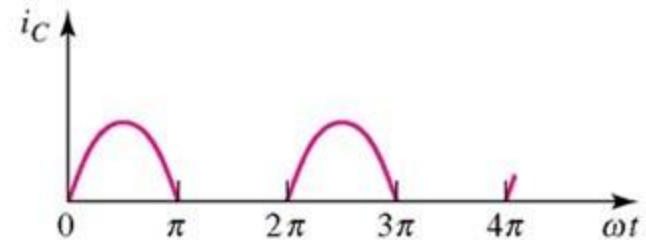Class B - The transistor conducts during one-half cycle of input signal



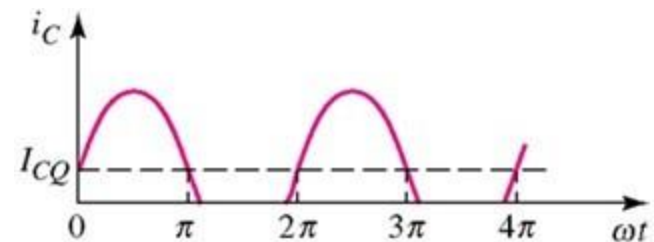Class AB - The transistor conducts for slightly more than half a cycle of input signal



Class	A	B	C	AB
Conduction Angle	360°	180°	Less than 90°	180 to 360°
Position of the Q-point	Centre Point of the Load Line	Exactly on the X-axis	Below the X-axis	In between the X-axis and the Centre Load Line
Overall Efficiency	Poor 25 to 30%	Better 70 to 80%	Higher than 80%	Better than A but less than B 50 to 70%
Signal Distortion	None if Correctly Biased	At the X-axis Crossover Point	Large Amounts	Small Amounts

Efficiency Ratings


- The **maximum theoretical efficiency** ratings of class-A, B, and C amplifiers are:

Amplifier	Maximum Theoretical Efficiency, η_{\max}
Class A	25%
Class B	78.5%
Class C	99%

Steps for Analysis of Power Amplifiers:


- ☐ Draw the Circuit Diagram of relevant type of Power Amplifier
- ☐ Draw the Graphical operating point representation
- ☐ Make DC analysis (AC components as 0) & Calculate ' P_{dc} '
- ☐ Make AC analysis (DC components as 0) & Calculate ' P_{ac} '
- ☐ Measure the Percentage Efficiency of the amplifier ($\% \eta$)
- ☐ Show the Power Dissipation
- ☐ Advantages and Disadvantages

Class A Amplifier

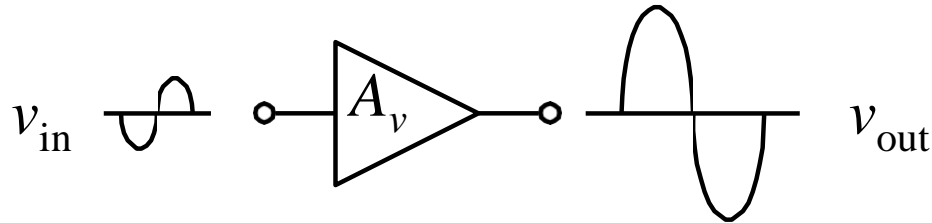


- v_{out} waveform \rightarrow **same shape** \rightarrow v_{in} waveform $+ \pi$ **phase shift.**
- The collector current is **nonzero** 100% of the time.
 - \rightarrow **inefficient**, since even with zero input signal, I_{CQ} is nonzero (i.e. transistor dissipates power in the rest, or quiescent, condition)

Class A Amplifier Classification

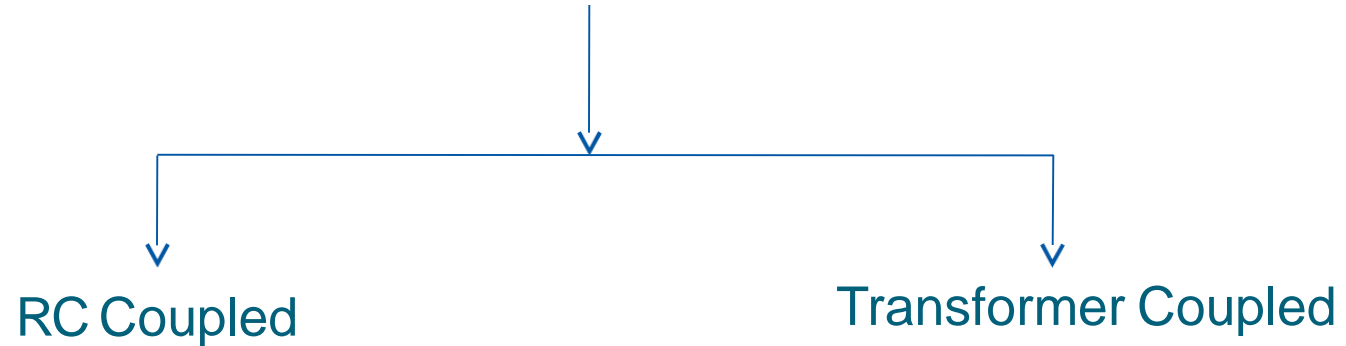


RC Coupled Class A Power Amplifier Analysis

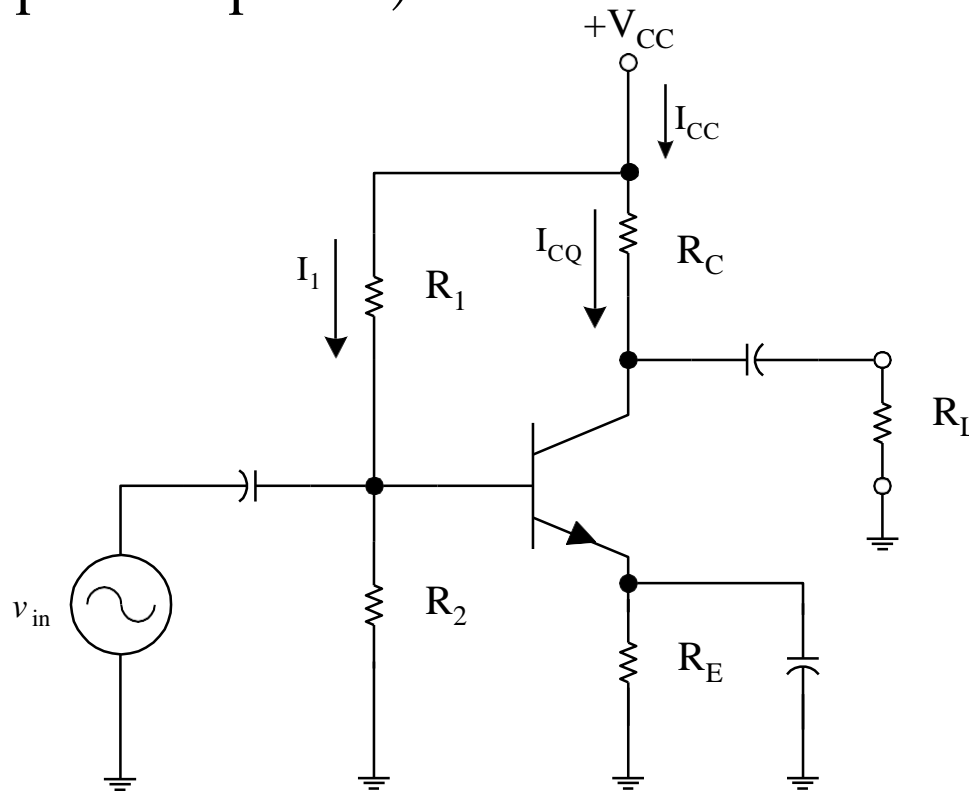Common-emitter (voltage-divider) configuration
(RC-coupled amplifier)



Typical Characteristic Curves for Class A Operation

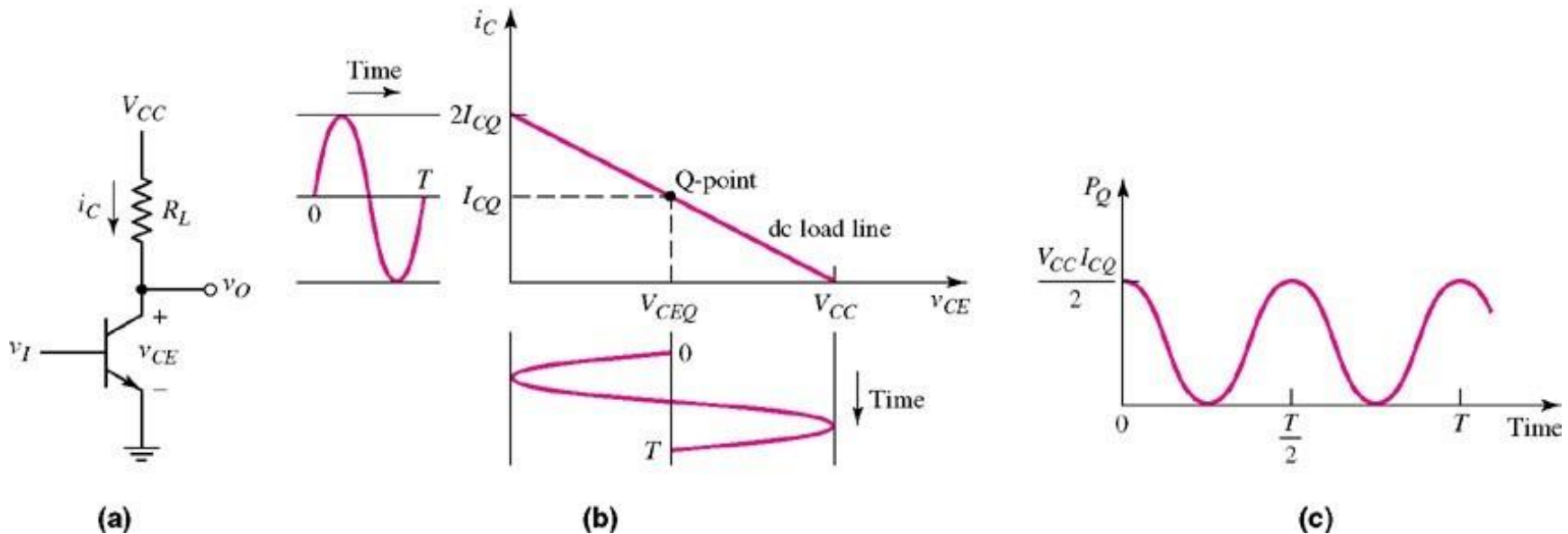- (a) Common-emitter amplifier,
- (b) dc load line (the Q point is at centre of the load line)
- (c) instantaneous power dissipation versus time in the transistor



DC Input Power


The total dc power, $P_i(dc)$, that an amplifier draws from the power supply :

$$P_i(dc) = V_{cc} I_{cc}$$

$$I_{cc} = I_{cq} + I_1$$

$$I_{cc} \approx I_{cq} \quad (I_{cq} \gg I_1)$$

$$P_i(dc) = V_{cc} I_{cq}$$

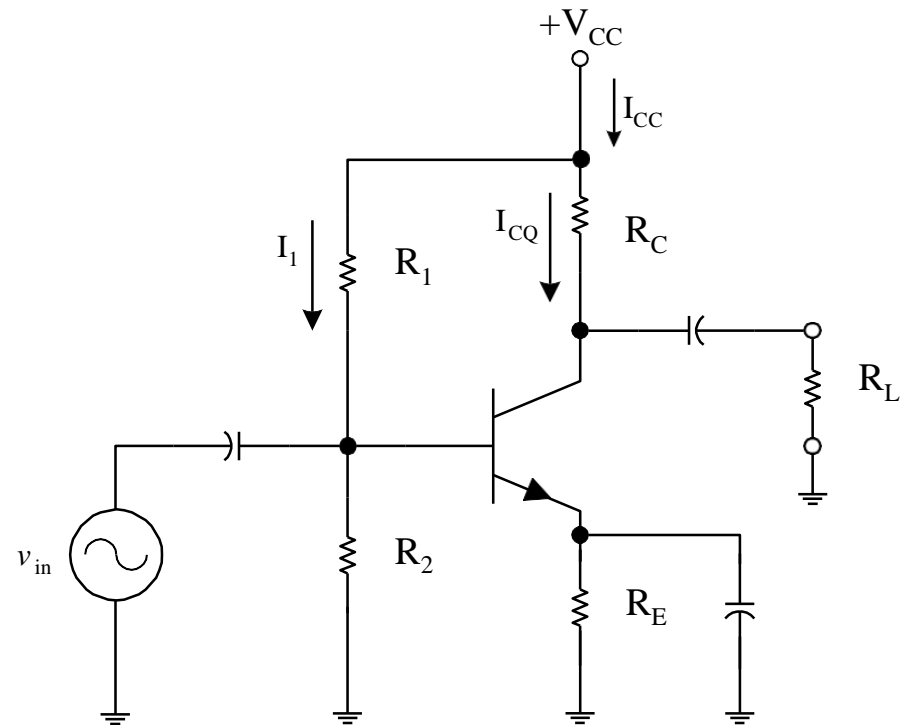

Note : That this equation is valid for most amplifier power analyses. We can rewrite for the above equation for the ideal amplifier as

$$P_i(dc) = V_{cc} I_{cq}$$

AC Output Power

$$P_o(ac) = i_{c(rms)} v_{o(rms)}$$


$$V_{o(rms)} = \frac{V_m}{\sqrt{2}} \quad I_{o(rms)} = \frac{I_m}{\sqrt{2}}$$

$$P_o(ac) = \frac{V_m}{\sqrt{2}} * \frac{I_m}{\sqrt{2}} = \frac{V_m * I_m}{2}$$

$$V_m = \frac{V_{pp}}{2} \quad I_m = \frac{I_{pp}}{2}$$

$$P_o(ac) = \frac{\frac{V_{pp}}{2} * \frac{I_{pp}}{2}}{2} = \frac{V_{pp} * I_{pp}}{8}$$
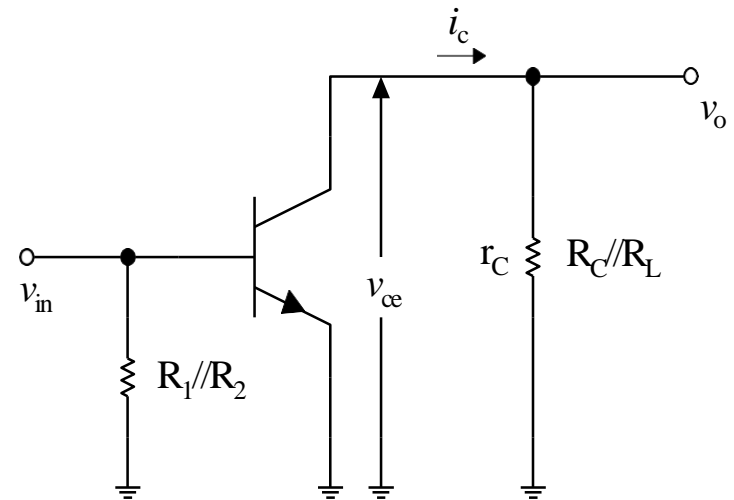
$$V_{pp} = \frac{V_{max} - V_{min}}{2} \quad I_{pp} = \frac{I_{max} - I_{min}}{2}$$



$$P_o(ac) = \frac{(V_{max} - V_{min}) * (I_{max} - I_{min})}{8}$$

Efficiency:

$$\% \eta = \frac{P_{ac}}{P_{dc}} * 100$$


$$P_o(ac) = \frac{(V_{max} - V_{min}) * (I_{max} - I_{min})}{8}$$

$$P_i(dc) = V_{CC} I_{CQ}$$

$$\% \eta = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{8 * V_{CC} * I_{CQ}} * 100$$

$$\% \eta = \frac{2 * V_{CC} * I_{CQ}}{8 * V_{CC} * I_{CQ}} * 100$$

$$\% \eta = 25\%$$

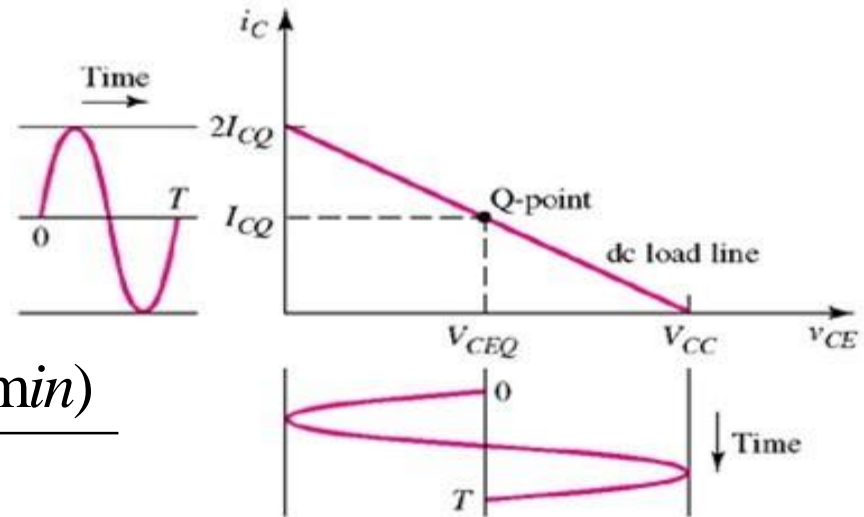

$$V_{max} = V_{CC} \text{ \& } V_{min} = 0$$

$$I_{max} = 2I_{CQ} \text{ \& } I_{min} = 0$$

⌘ **Advantages:**



- 1) Circuit is Simple to Design
- 2) Less no. of Components

⌘ **Dis-Advantages:**

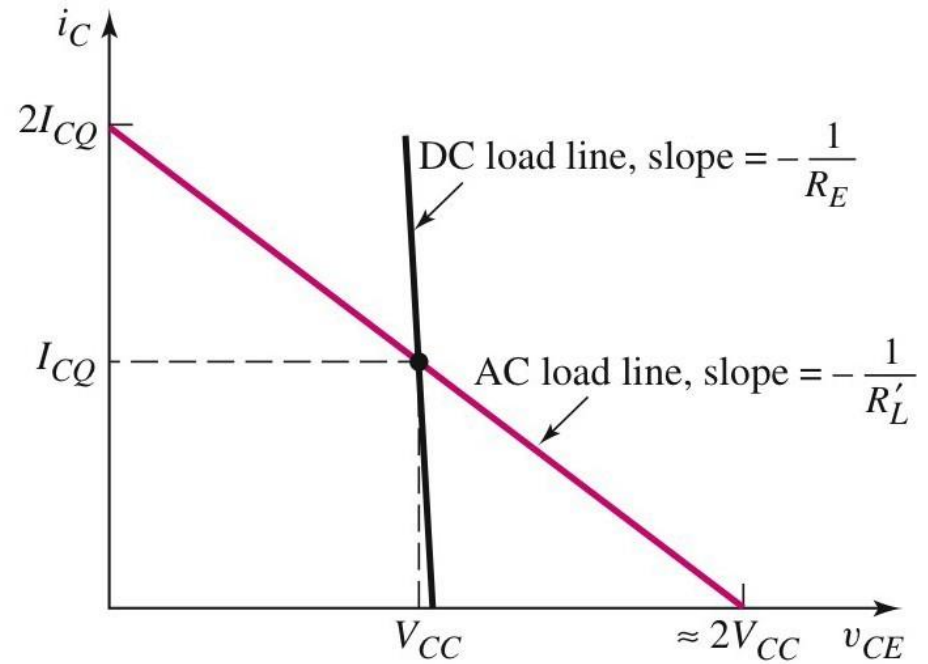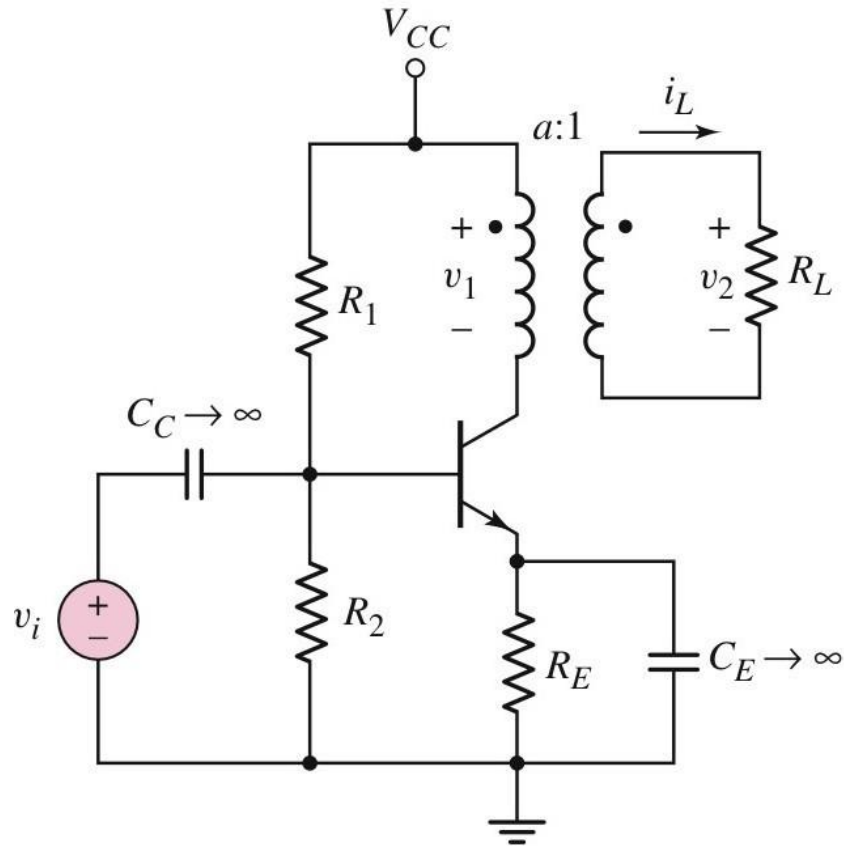- 1) Load Resistor is directly connected to collector. This causes considerable wastage of Power
- 2) Power Dissipation is More
- 3) Efficiency is very poor, due to large power Dissipation


Transformer Coupled Amplifier

- The theoretical maximum efficiency of a basic RC-coupled class-A amplifier is limited to 25%.
- In practical circuit, the efficiency is less than 25%.
- Used for output power of about 1 W only.
- Transformer coupling can increase the maximum efficiency to 50%
- Disadvantage of transformer coupling – expensive & bulky.



Neglecting transformer resistance and assuming R_E is small;

$$V_{CEQ} \cong V_{CC}$$

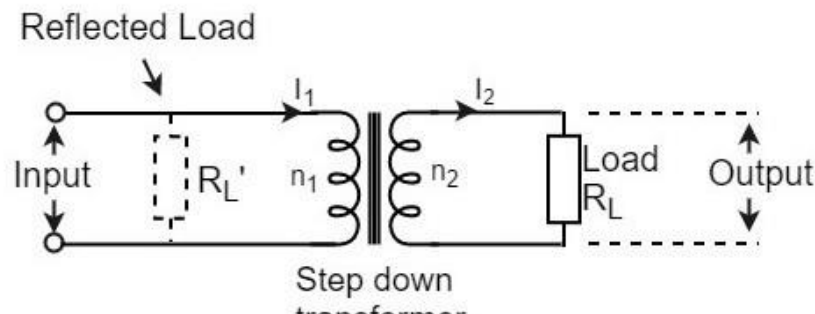

$$\frac{V_1}{V_2} = \frac{n_1}{n_2} \text{ and } \frac{I_1}{I_2} = \frac{n_1}{n_2}$$

Or

$$V_1 = \frac{n_1}{n_2} V_2 \text{ and } I_1 = \frac{n_1}{n_2} I_2$$

Hence

$$\frac{V_1}{I_1} = \left(\frac{n_1}{n_2} \right)^2 \frac{V_2}{I_2}$$

But $V_1/I_1 = R_L' =$ effective input resistance

And $V_2/I_2 = R_L =$ effective output resistance

Therefore,

$$R_L' = \left(\frac{n_1}{n_2} \right)^2 R_L = n^2 R_L$$

Where

$$n = \frac{\text{number of turns in primary}}{\text{number of turns in secondary}} = \frac{n_1}{n_2}$$

A power amplifier may be matched by taking proper turn ratio in step down transformer.

→ DC Input Power

The total dc power, $P_i(dc)$, that an amplifier draws from the power supply :

$$P_i(dc) = V_{cc} I_{cc}$$

$$I_{cc} \approx I_{cq} \quad (I_{cq} \gg I_1)$$

$$P_i(dc) = V_{cc} I_{cq}$$

Note : That this equation is valid for most amplifier power analyses. We can rewrite for the above equation for the ideal amplifier as

$$P_i(dc) = V_{cc} I_{cq}$$

i_c

→ AC Output Power

$$P_o(ac) = i_{1(rms)} v_{1(rms)} \quad P_o(ac) = i_{2(rms)} v_{2(rms)}$$

At Primary side A.C power generated:

$$P_o(ac) = i_{1(rms)} v_{1(rms)} = I_{1rms}^2 R'_L = \frac{V_{1rms}^2}{R'_L}$$

i_c

$$P_o(ac) = \frac{V_{1m}}{\sqrt{2}} * \frac{I_{1m}}{\sqrt{2}} = \frac{V_{1m} * I_{1m}}{2}$$

$$V_m = \frac{V_{pp}}{2} \quad I_m = \frac{I_{pp}}{2}$$

$$V_{pp} = \frac{V_{max} - V_{min}}{2}$$

$$I_{pp} = \frac{I_{max} - I_{min}}{2}$$

⌘ We consider an idea Transformer, means Power delivered on primary side is equal to the secondary side load, and the values of currents and voltages are similar.


$$P_o(ac) = \frac{\frac{V_{pp}}{2} * \frac{I_{pp}}{2}}{2} = \frac{V_{pp} * I_{pp}}{8}$$

$$P_o(ac) = \frac{(V_{max} - V_{min}) * (I_{max} - I_{min})}{8}$$

$$P_i(dc) = V_{cc} I_{cq}$$

Efficiency:
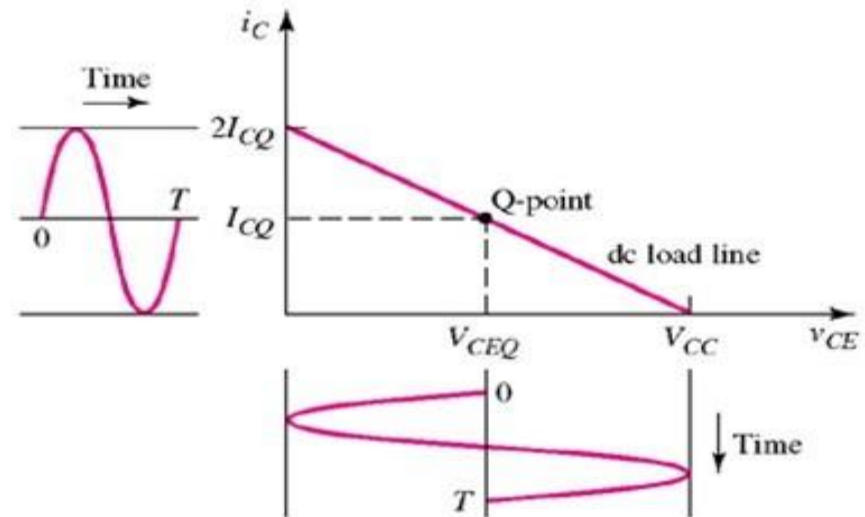
$$\% \eta = \frac{P_{ac}}{P_{dc}} * 100$$



$$P_o(ac) = \frac{(V_{max} - V_{min}) * (I_{max} - I_{min})}{8}$$

$$P_i(dc) = V_{CC} I_{CQ}$$

$$V_{max} = 2V_{CC} \text{ \& } V_{min} = 0$$

$$I_{max} = 2I_{CQ} \text{ \& } I_{min} = 0$$

$$\% \eta = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{8 * V_{CC} * I_{CQ}} * 100$$

$$\% \eta = 50\%$$

$$\% \eta = \frac{4 * V_{CC} * I_{CQ}}{8 * V_{CC} * I_{CQ}} * 100$$

Power Dissipation:

$$P_d = P_{DC} - P_{AC}$$

- ─ In case of Class A amplifiers, Power Dissipation is maximum when no input signal is applied.

Advantages:

- 1) Efficiency be somewhat high compared to series fed Class A
- 2) Impedance matching is required for maximum power transfer is possible

Dis-Advantages:

- 1) Due to Transformer, the circuit becomes bulkier, heavier and costlier compared to series fed type
- 2) Frequency response of the circuit is poor
- 3) Circuit is complicated to design and implementation compared to series fed type

Class A advantages:

- No cross over distortion
- No switching distortion
- Lower harmonic distortion in the voltage amplifier
- Lower harmonic distortion in the current amplifier
- No signal dependent distortion from the power supply
- Constant and low output impedance
- Simpler design

Class A dis-advantages:

- Low Efficiency
- Power Dissipation more
- Wastage of Power

Example

Calculate the input power [$P_{i(dc)}$], output power [$P_{o(ac)}$], and efficiency [η] of the amplifier circuit for an input voltage that results in a base current of 10mA peak.

$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{20V - 0.7V}{1k\Omega} = 19.3mA$$

$$I_{CQ} = \beta I_B = 25(19.3mA) = 482.5mA \cong 0.48A$$

$$V_{CEQ} = V_{CC} - I_C R_C = 20V - (0.48A)(20\Omega) = 10.4V$$

$$I_{c(sat)} = \frac{V_{CC}}{R_C} = \frac{20V}{20\Omega} = 1000mA = 1A$$



$$V_{CE(cutoff)} = V_{CC} = 20V$$

$$I_{C(peak)} = \beta I_{b(peak)} = 25(10mA \text{ peak}) = 250mA \text{ peak}$$

$$P_{o(ac)} = \frac{I_{C(peak)}^2}{2} R_C = \frac{(250 \times 10^{-3} A)^2}{2} (20\Omega) = 0.625W$$



$$P_{i(dc)} = V_{CC} I_{CQ} = (20V)(0.48A) = 9.6W$$
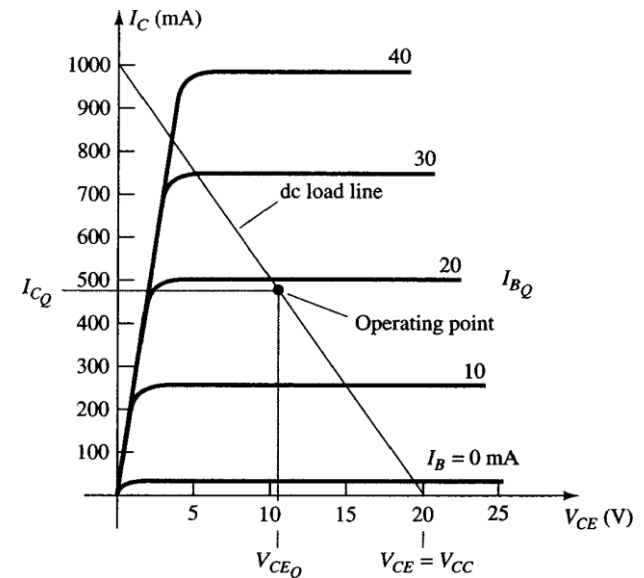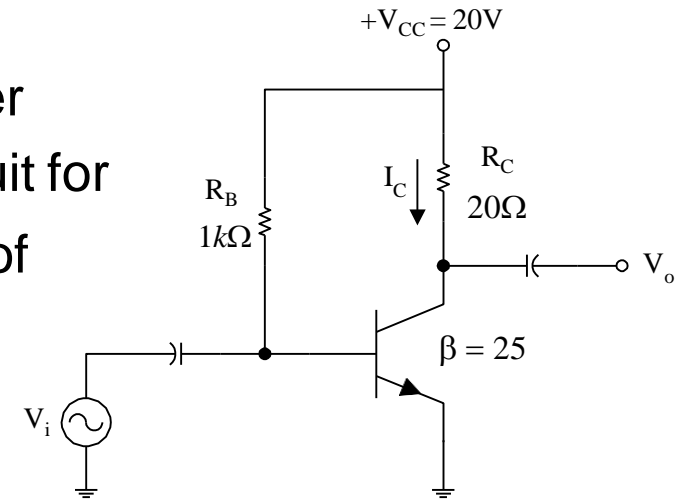
$$\eta = \frac{P_{o(ac)}}{P_{i(dc)}} \times 100\% = 6.5\%$$




Class B Power Amplifier

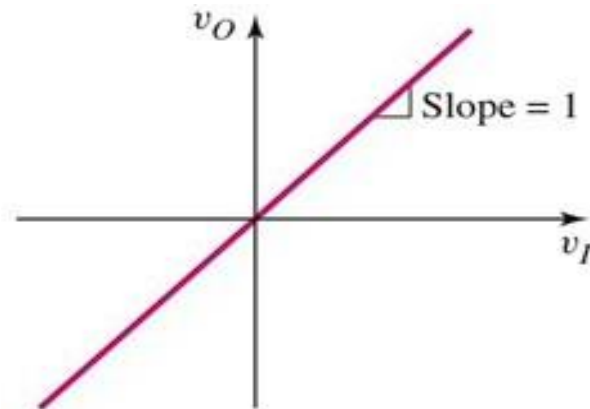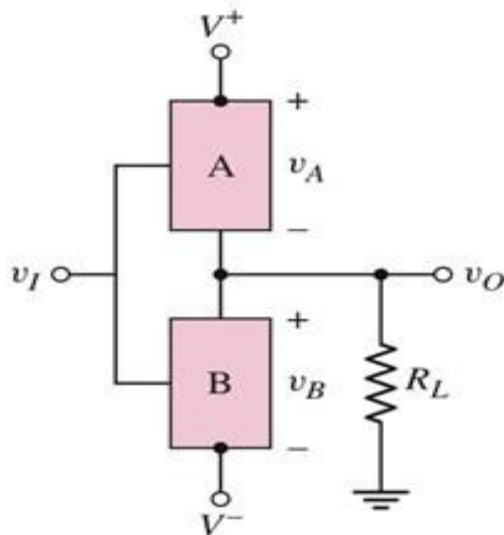
- Consists of **Push-Pull** & **complementary pair** electronic devices
- One conducts for **one half cycle** of the input signal and the other **conducts for another half of the input signal**
- When the input is zero, both devices are off, the bias currents are zero and the output is zero.
- Ideal voltage gain is unity



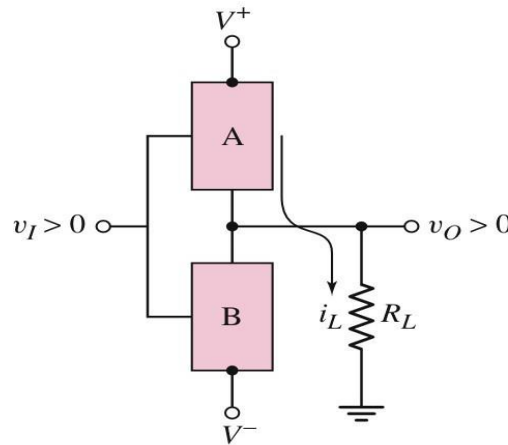
- For input larger than zero, A turn ON and supplies current to the load.



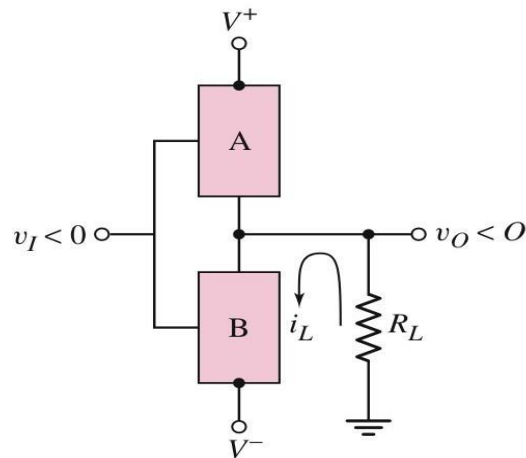- For input less than zero, B turn ON and sinks current from the load



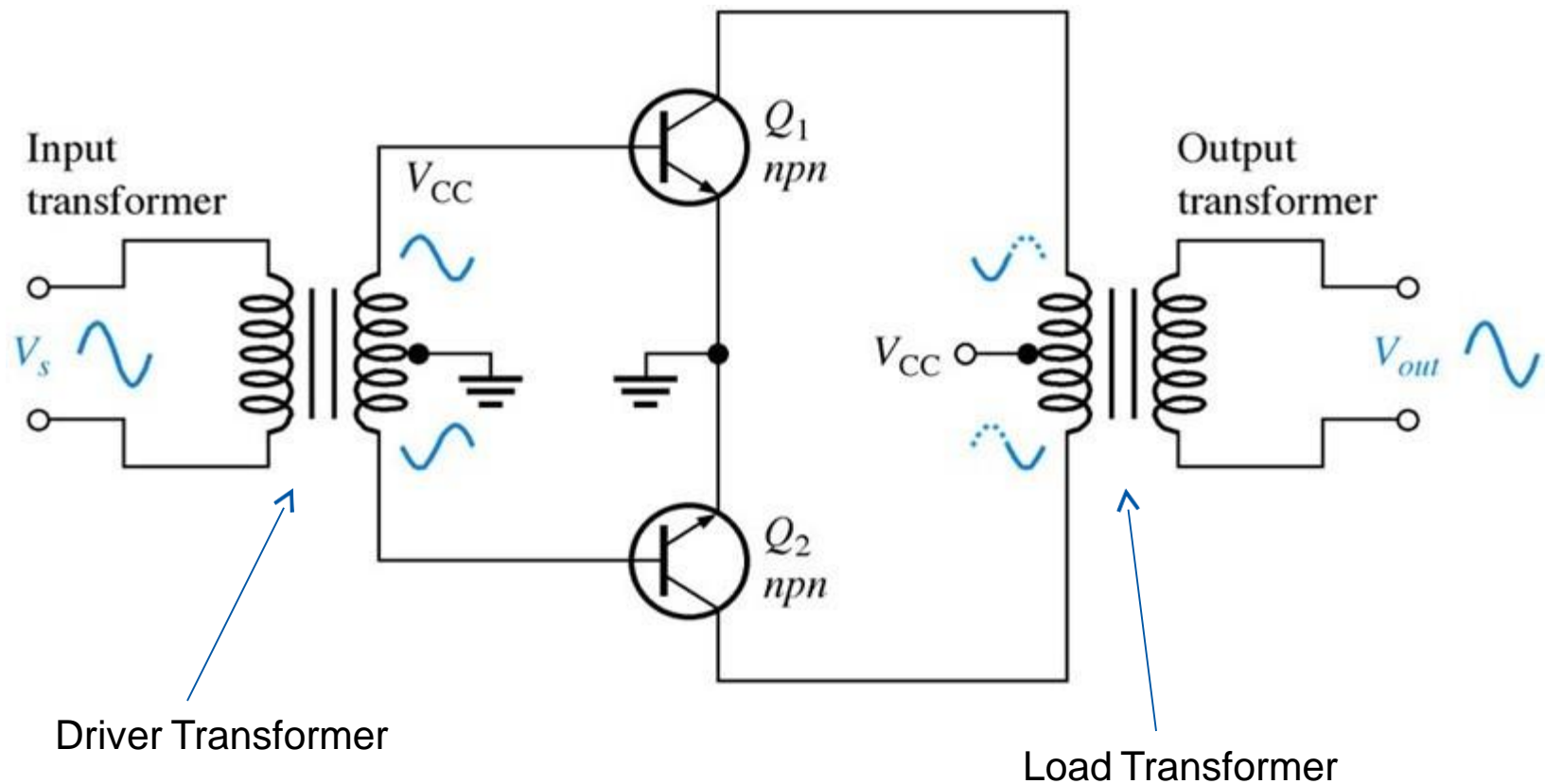Class-B transformer coupled push pull amplifier



→ DC Input Power


- DC biasing point is on the X-axis so the $V_{ceq} = V_{CC}$. And I_{ceq} becomes 0. hence Q-point ($V_{CC}, 0$).

- Each Transformer output is an Half-rectified Waveform. Then peak value of the output current is the average d.c current

$$I_1(dc) = \frac{I_m}{\pi} \quad I_2(dc) = \frac{I_m}{\pi}$$

$$I(dc) = \frac{I_m}{\pi} + \frac{I_m}{\pi} = \frac{2I_m}{\pi}$$
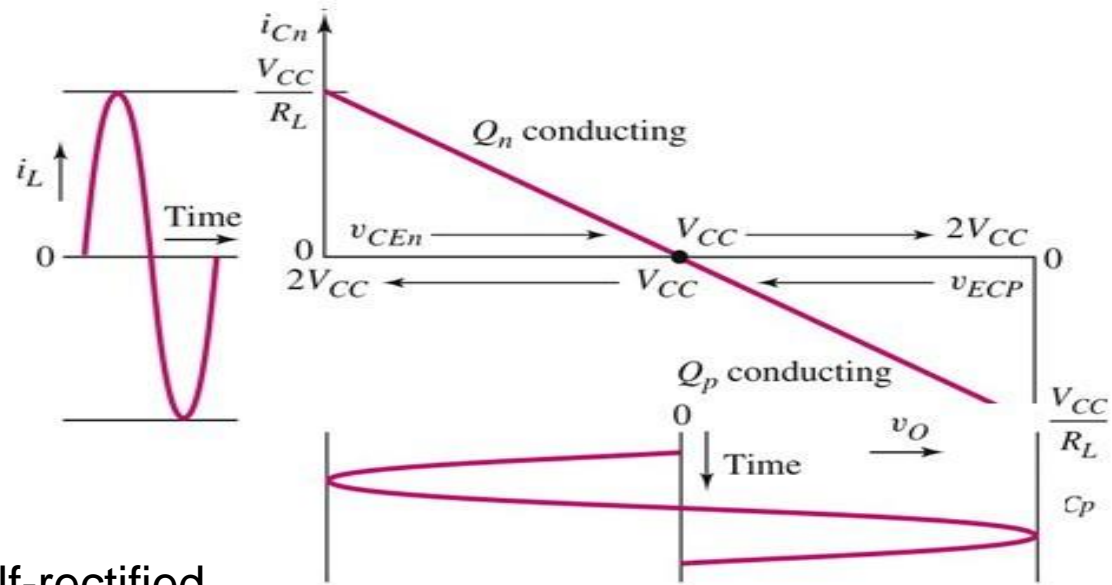
$$P(dc) = V_{CC} I_{dc} = \frac{2}{\pi} V_{CC} I_m$$



→ AC Output Power

$$P_o(ac) = i_{1(rms)} v_{1(rms)} \quad P_o(ac) = i_{2(rms)} v_{2(rms)}$$

At Primary side A.C power generated:

$$P_o(ac) = i_{1(rms)} v_{1(rms)} = I_{1rms}^2 R_L' = \frac{V_{1rms}^2}{R_L'}$$

$$P_o(ac) = \frac{V_m}{\sqrt{2}} * \frac{I_m}{\sqrt{2}} = \frac{V_m * I_m}{2} = \frac{I_m^2 R_L'}{2} = \frac{V_m^2}{2 R_L'}$$

Efficiency:

$$\% \eta = \frac{P_{ac} * 100}{P_{dc}}$$

$$P_o(ac) = \frac{V_m * I_m}{2}$$


$$P(dc) = \frac{2}{\pi} V_{CC} I_m$$

$$\% \eta = \frac{\pi * V_m * 100}{4 V_{CC}}$$

$$\% \eta = \frac{\pi * V_{CC} * 100}{4 V_{CC}}$$

- $V_m = V_{CC}$

$$\% \eta = 78.5\%$$

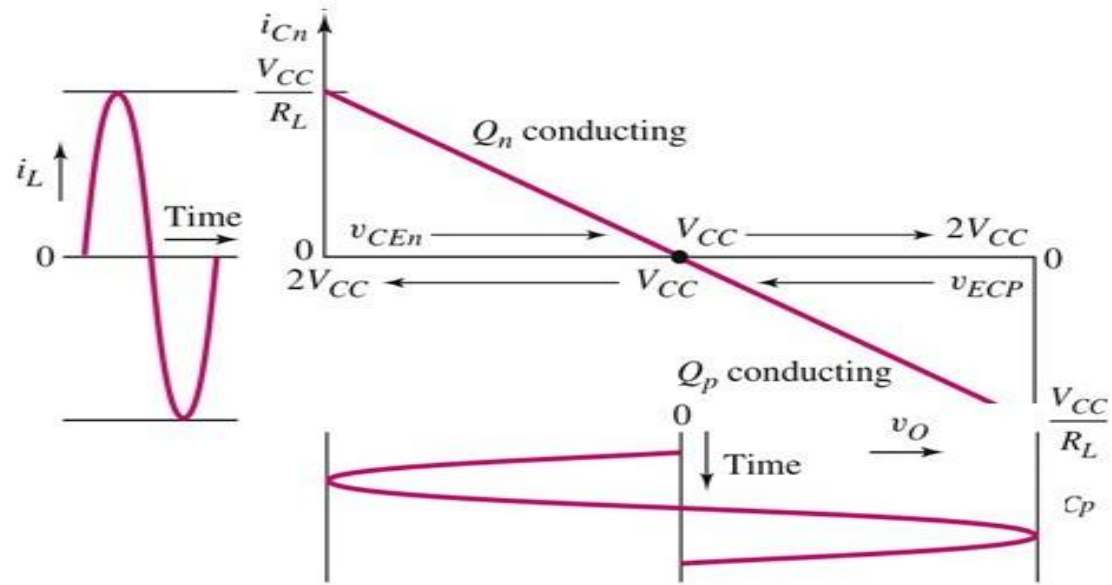

Power Dissipation:

$$P_d = P_{DC} - P_{AC}$$

$$P_d = \frac{2}{\pi} V_{CC} I_m - \frac{V_m^* I_m}{2}$$

- In case of Class A amplifiers, Power Dissipation is maximum when no input signal is applied. But in Case of Class B, when input is 0 then $V_m=0$. Hence Power dissipation is very less compared to Class A.



Advantages:



- 1) Efficiency is much higher than Class A operation.
- 2) When there is no input signal, the power dissipation is zero.
- 3) Harmonics get cancelled. This reduces the harmonic distortion.
- 4) Ripples present in supply voltage also get eliminated.
- 5) Due to the Transformer impedance Matching is possible.

Dis-Advantages:

- 1) Frequency response of the circuit is poor
- 2) Center Tap transformers are necessary.
- 3) Transformers make the circuit bulky and hence costlier

Complimentary Symmetry Class B Circuit

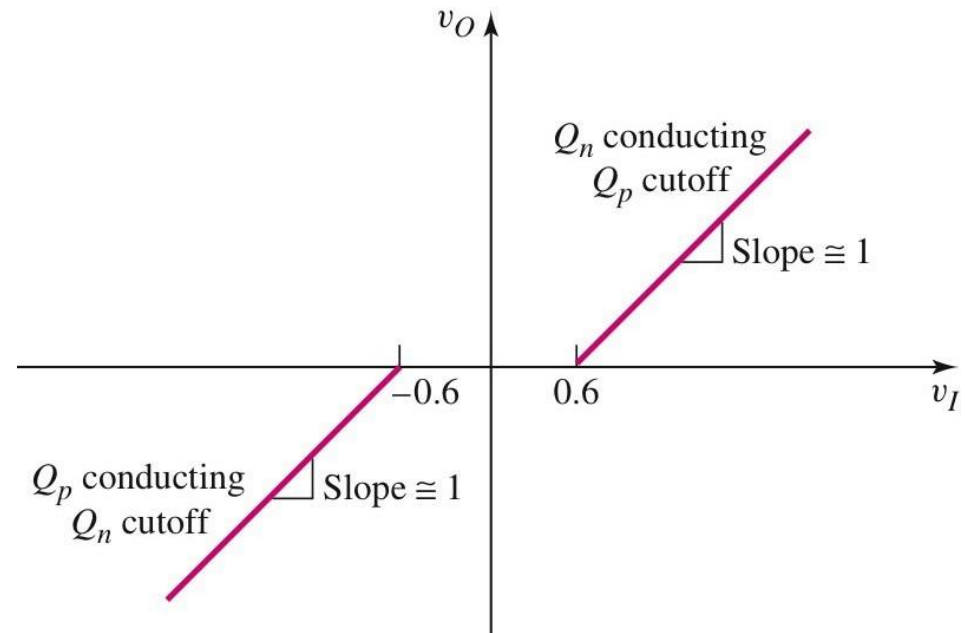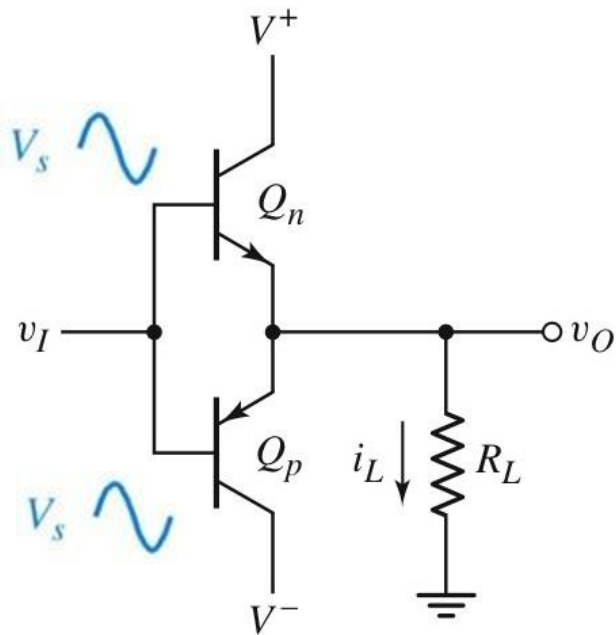

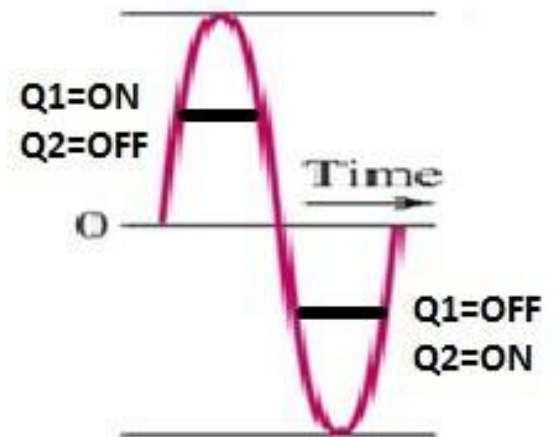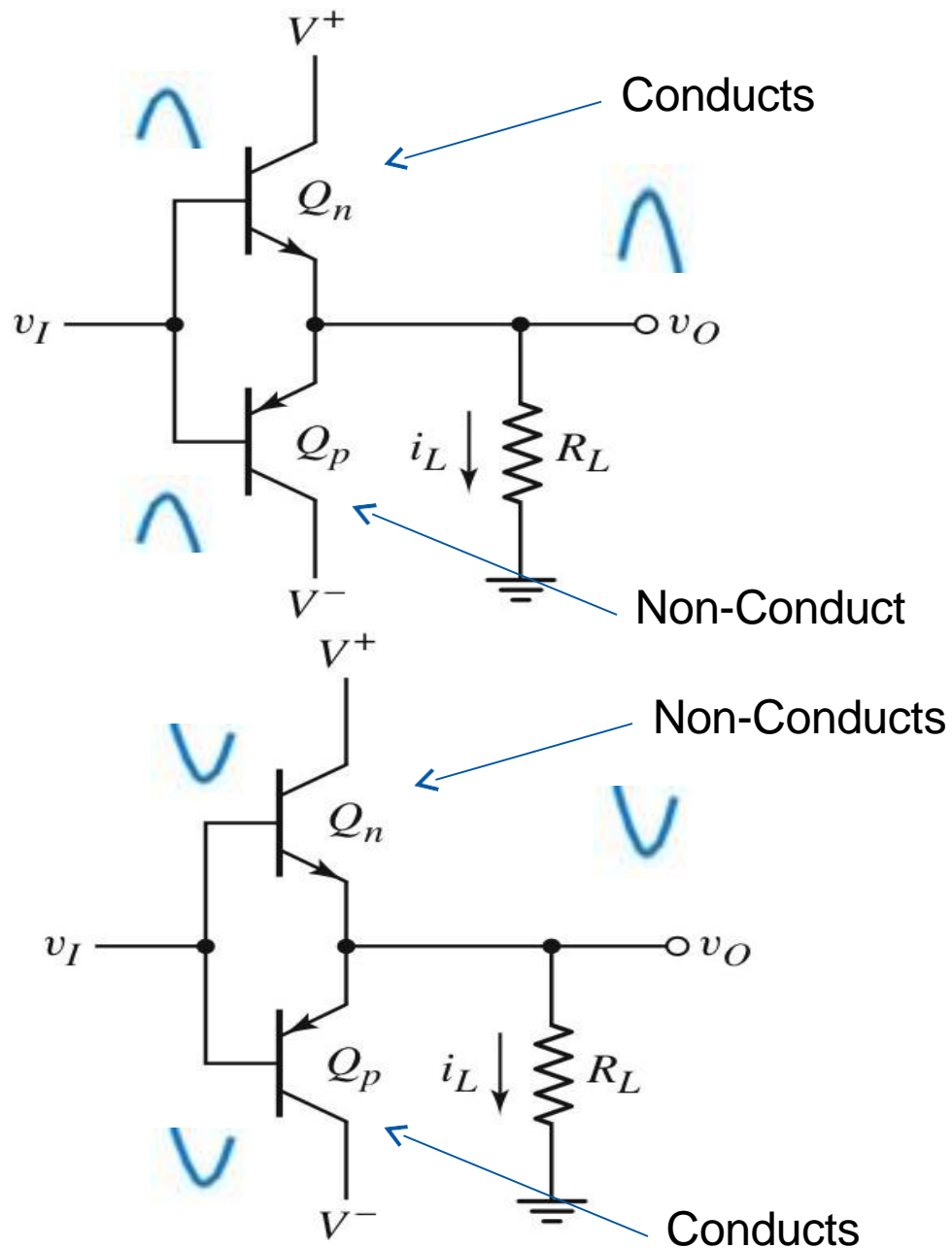


Advantages:

- 1) As the circuit is transformer less, its weight, size and cost are less.
- 2) Due to the common collector configuration, impedance matching is possible.
- 3) Frequency response of the circuit is improved due to transformer less Class B amplifier circuit

Dis-Advantages:



- 1) Circuit needs two separate voltage supplies
- 2) Output suffers cross-over distortion

CROSSOVER DISTORTION

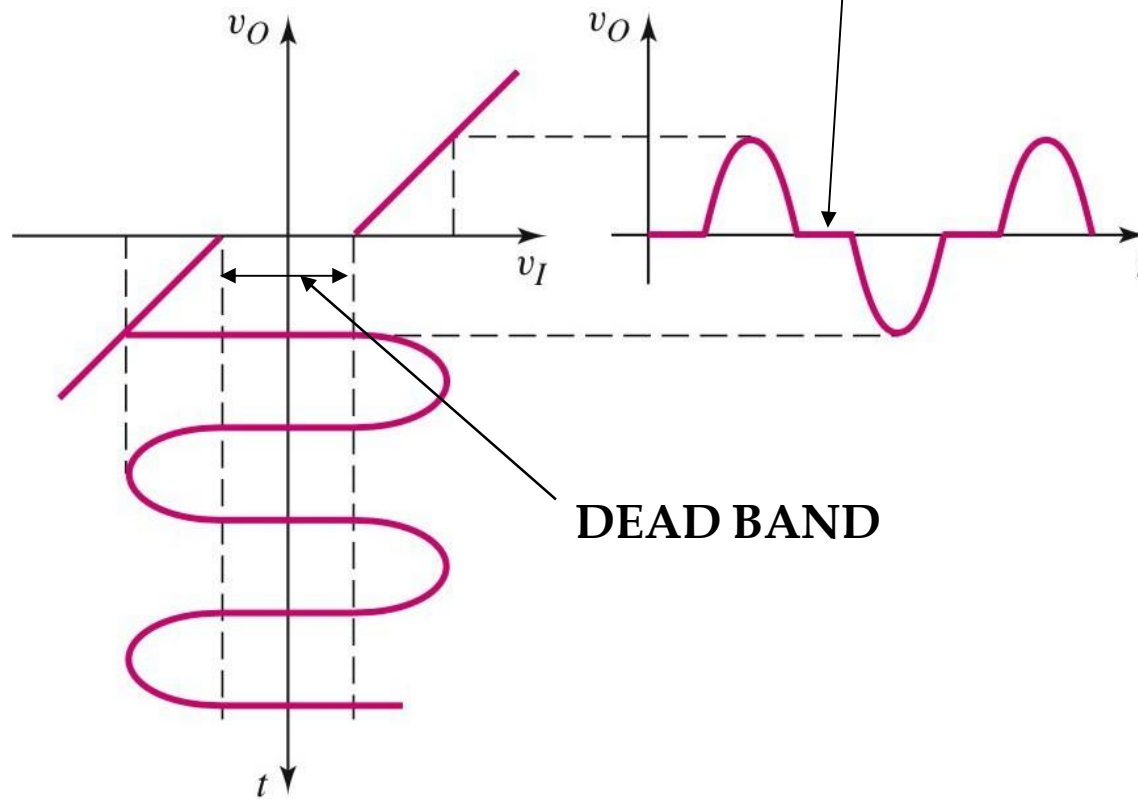


→ Cross-over distortion free circuits

- Push-Pull Distortion Less circuit:

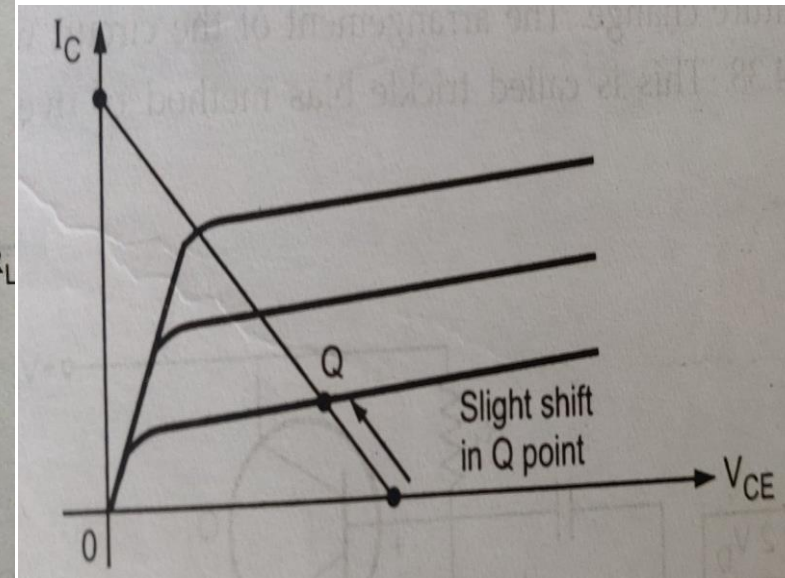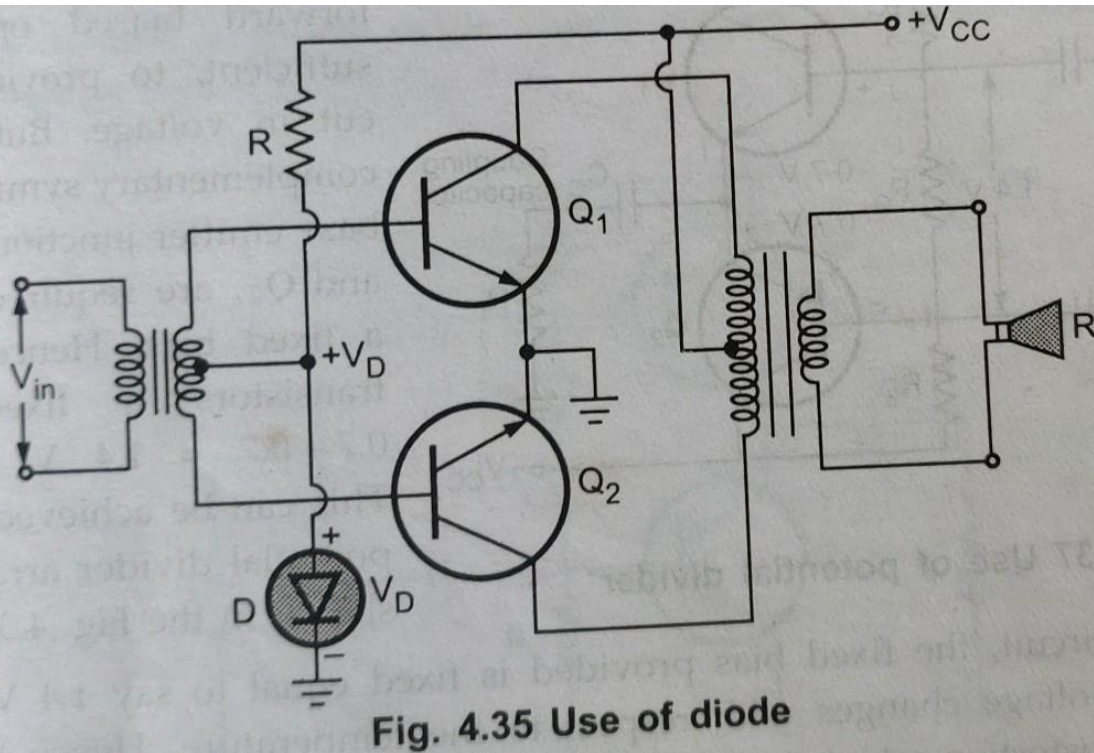


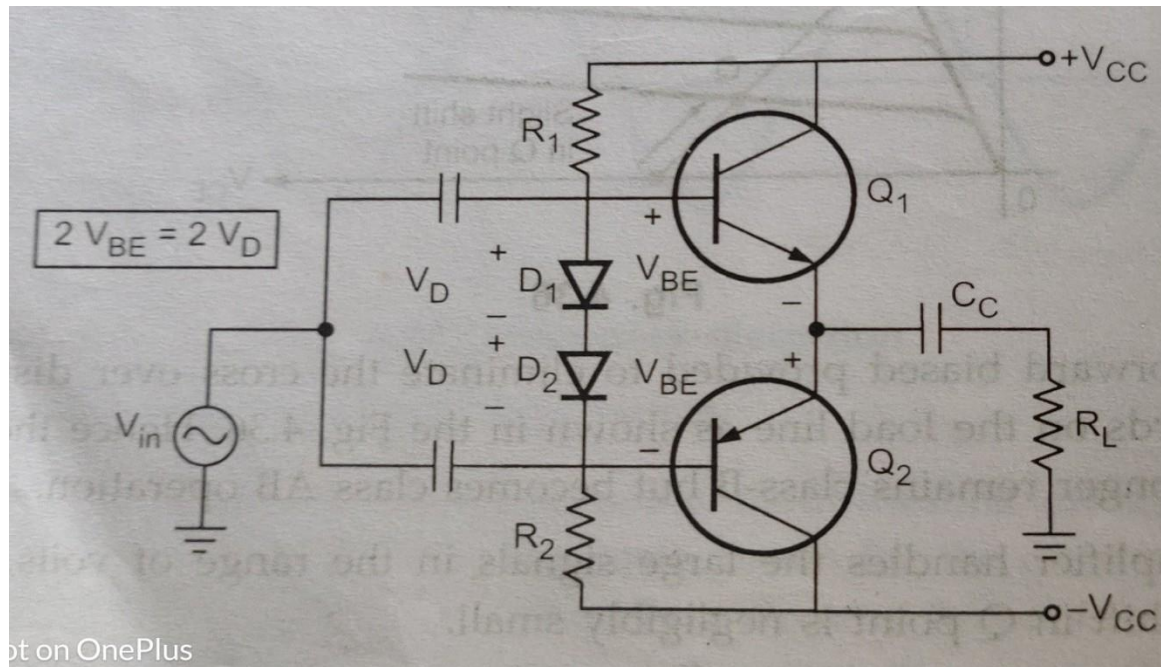- Complementary Push-Pull Distortion Less circuit:




Class AB Power Amplifier


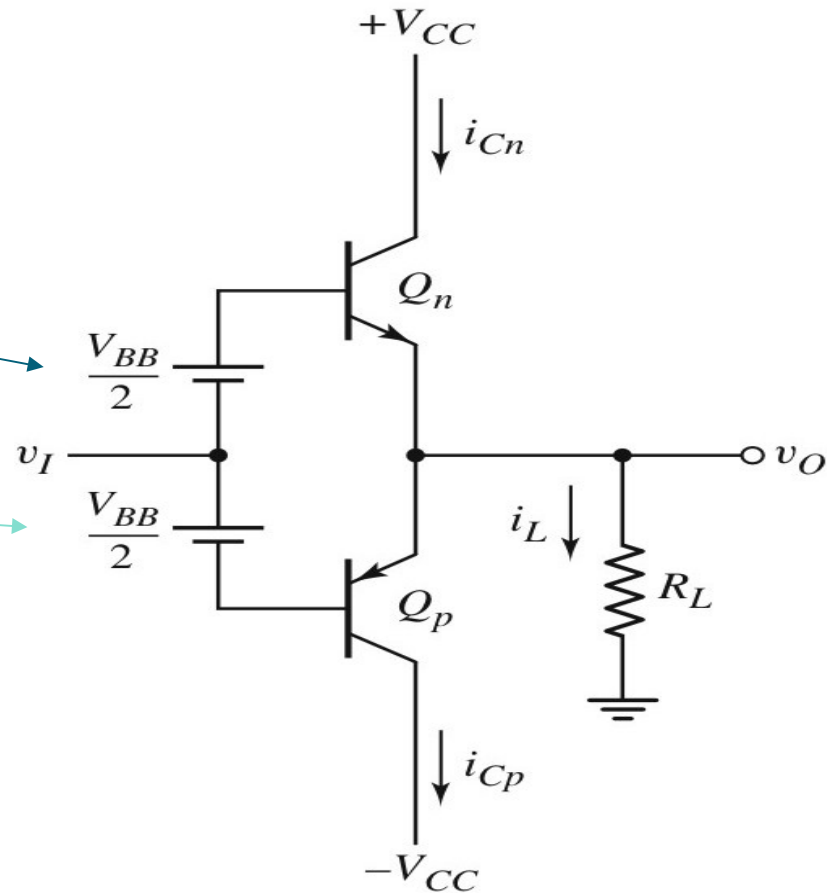
Small quiescent bias
on each output
transistor to
eliminate *crossover*
distortion




Class AB Voltage Transfer Curve

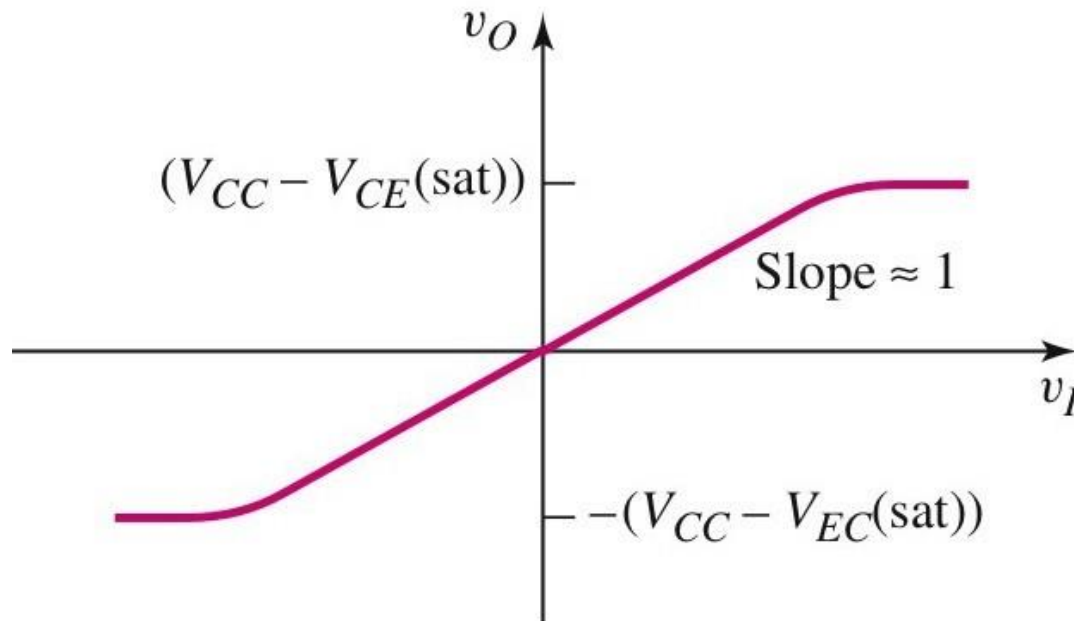



Class C Power Amplifier

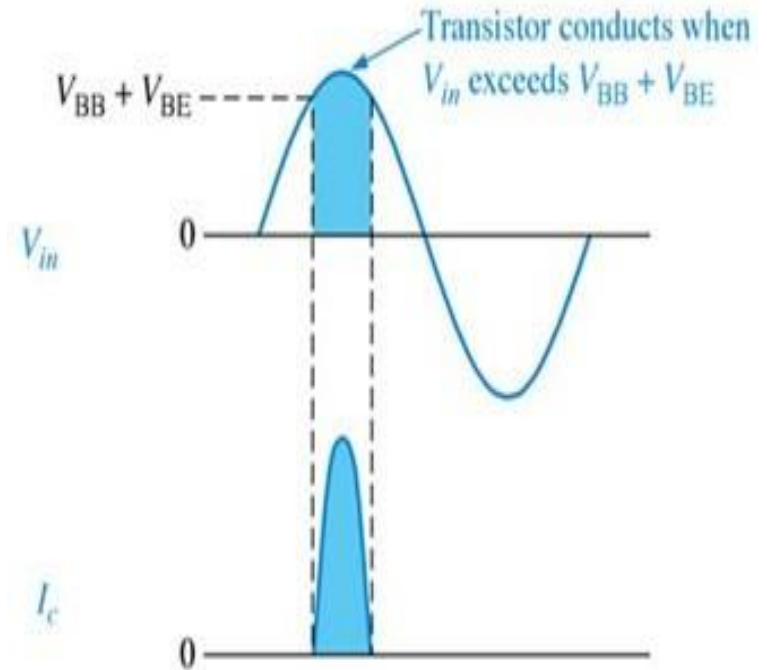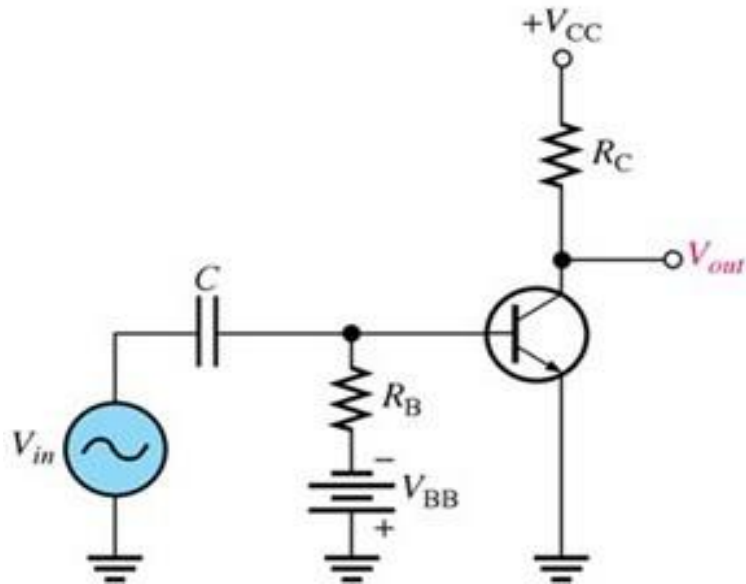

Load line Operation:

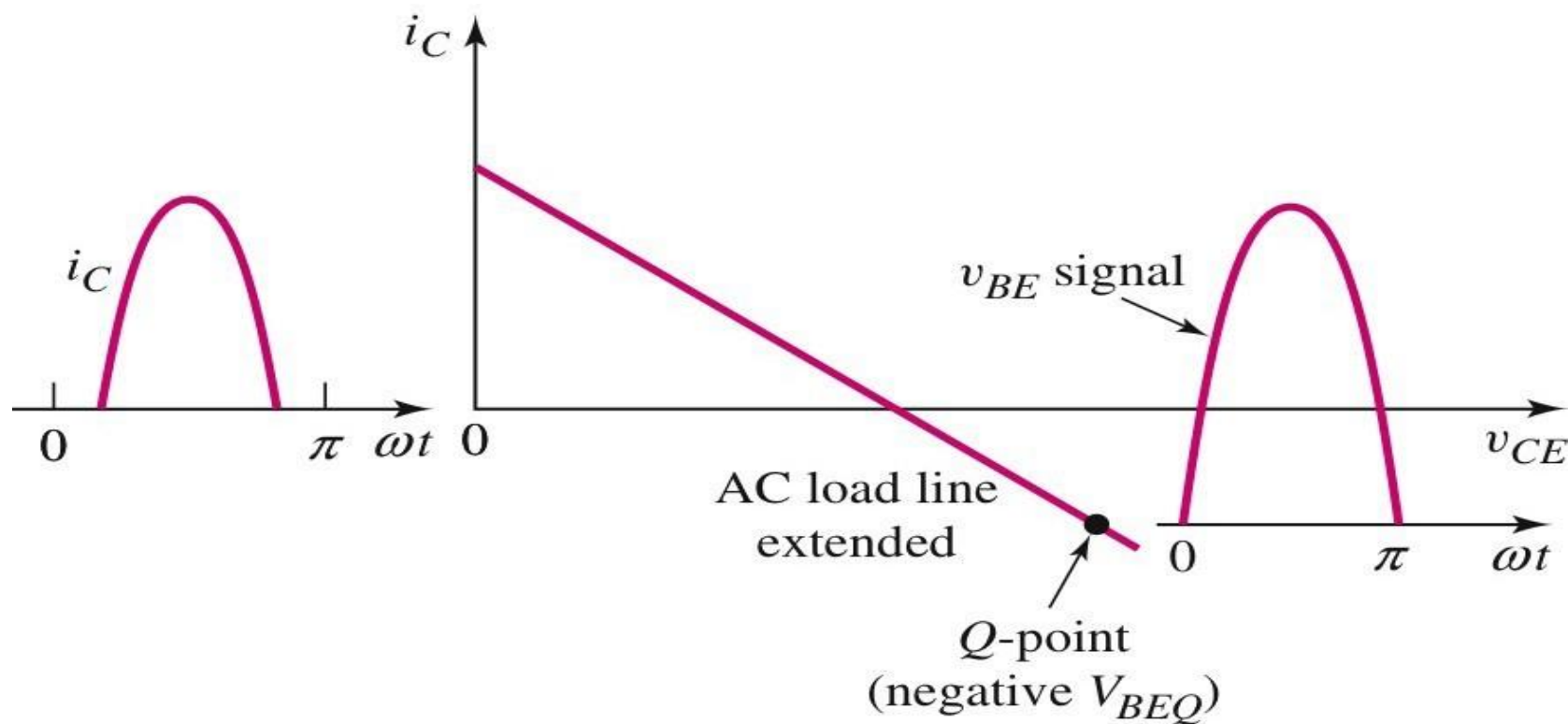

Collector Currents & Output Current

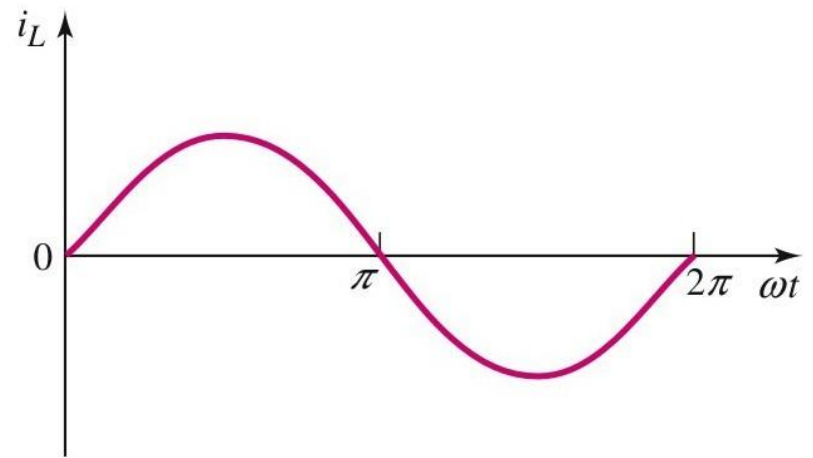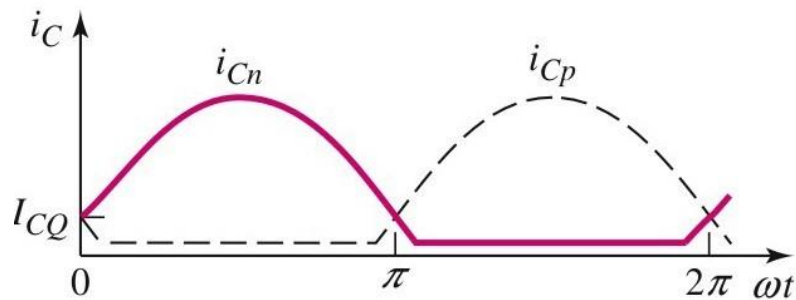

$$i_{Cn} = i_L + i_{Cp}$$


Comparison of Amplifiers

Class	A	B	C	AB
Operating Cycle	360°	180°	Less than 180°	180° to 360°
Position of Q-Point	Center of Load Line	On X-axis	Below X-axis	In between X-axis to center of Load line
Efficiency	Poor, 25% to 50%	Better, 78.5%	High	In between 78.5% to 50%
Distortion	No	Present	Highest	Present


Distortion in Amplifiers

□ Amplifier Distortion :

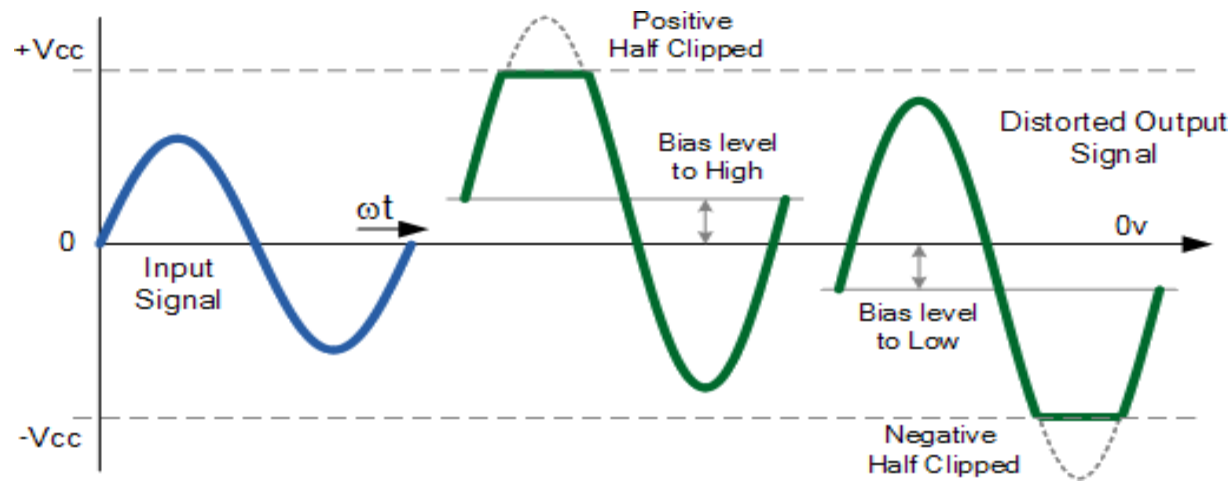
Amplifier Distortion can take on many forms such as Amplitude, Frequency and Phase Distortion due to Clipping




Amplitude Distortion :

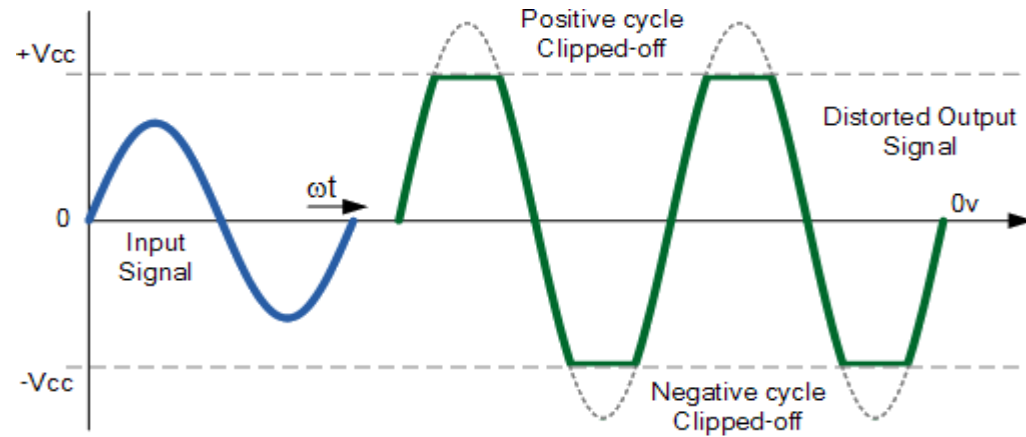

Frequency Distortion :

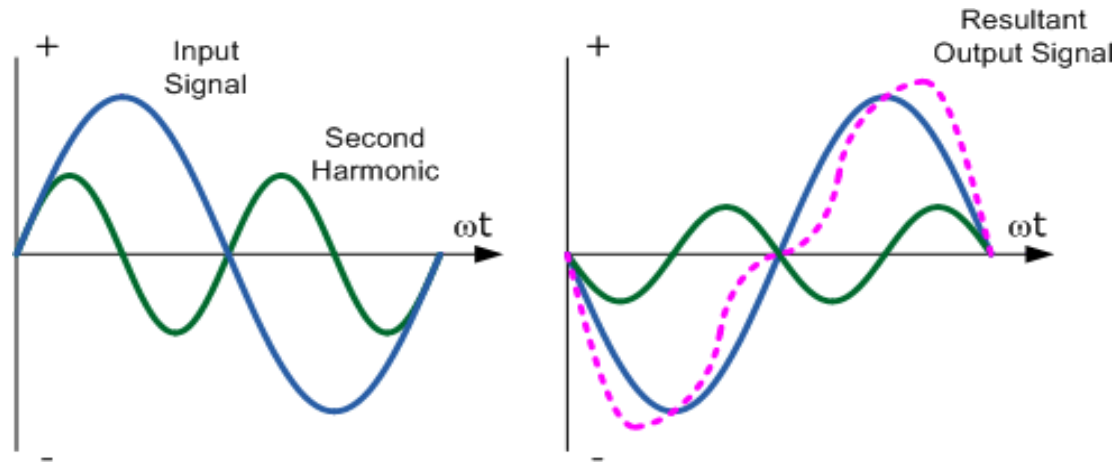

Phase Distortion :

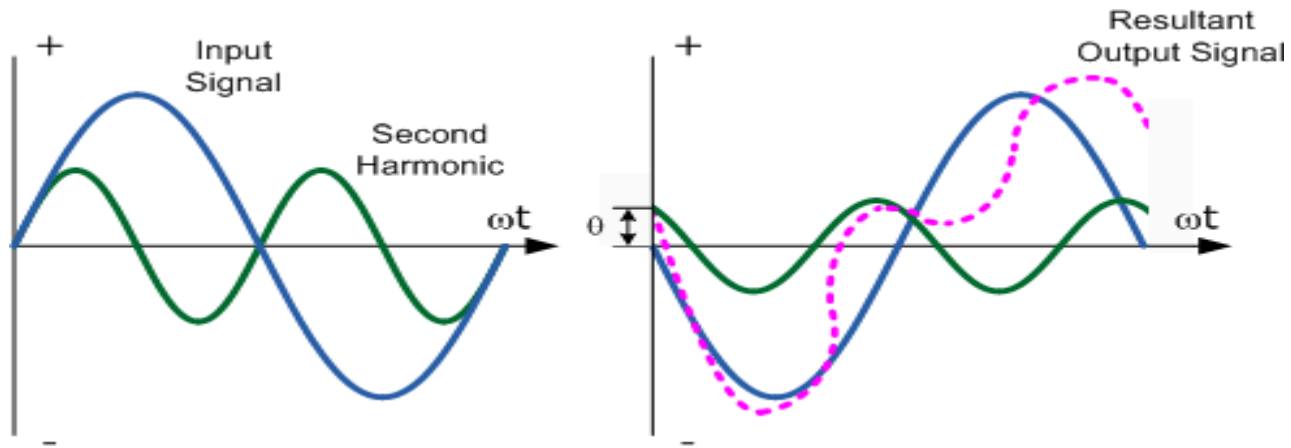

GATE Questions with Solutions

Example:

5.02. Calculate the effective resistance seen looking into the primary of a 15 : 1 transformer connected to an 8Ω load

- (A) $2k\Omega$ (B) $1.8k\Omega$
(C) $3k\Omega$ (D) $4k\Omega$

Sol. $R_L^1 = \left(\frac{N_1}{N_2} \right)^2 R_L = (15)^2 8$

$R_L^1 = 1.8k\Omega$ Choice (B)

Examples:

- 5.03. Calculate the total harmonic distortion for the amplitude components as $A_1 = 1.5V$, $A_2 = 0.25$, $A_3 = 0.05$

Sol. $D_2 = \frac{|A_2|}{|A_1|} = \frac{0.25}{1.5} = \frac{1}{6}$

$$D_3 = \frac{|A_3|}{|A_1|} = \frac{0.05}{1.5} = \frac{1}{30}$$

$$THD = \sqrt{\left(\frac{1}{6}\right)^2 + \left(\frac{1}{30}\right)^2} = 0.17\%$$

- 5.04. Calculate the efficiency of a class 'B' amplifier for a supply voltage of 24 volts with peak voltage of 8 volts.
(A) 26.18% (B) 35.62%
(C) 40.25% (D) 52.36%

Scanned with CamScanner

Sol. $\eta = 78.54 \frac{V_L(p)}{V_{cc}} \% = 78.54 \times \frac{8}{24}$
 $= 26.18 \text{ volts}$ Choice (A)

3. The ac power output of a class A amplifier is 4w. If the collector efficiency is 45%, what is the power rating of transistor?

(A) $\geq 8.9\text{w}$ (B) $< 8.9\text{w}$

(C) $\geq 4\text{w}$ (D) $< 4\text{w}$

Sol. $P_{o(ac)} = 4\text{w}$

$$\eta = 45\% = 0.45$$

$$\Rightarrow \eta = \frac{P_{o(ac)}}{P_{in(dc)}}$$

$$P_{in(dc)} = \frac{P_{o(ac)}}{\eta} = \frac{4}{0.45} = 8.9\text{W}$$

4 $P_{Dmax} \geq P_{in(dc)}$ for class A.

$$P_{Dmax} \geq 8.9\text{W}$$

Choice (A)

4. A class B push-pull amplifier uses 15V dc supply, with sinusoidal input, a max peak to peak of 24V is desired across a load of 100Ω . What is the power dissipated by each transistor?

- (A) 426mW (B) 213mW
(C) 1.146W (D) 0.72W

Sol. Peak to peak value of o/p $V_{PP} = 24V$

$$\text{Peak value of o/p } V_P = \frac{24}{2} = 12V$$

$$R_L = 100\Omega$$

$$\text{Peak value of o/p current } I_P = V_P / R_L$$

$$\Rightarrow I_P = \frac{12}{100} = 0.12A$$

Dc current drawn from V_{CC} supply is

$$I_{dc} = \frac{2I_P}{\pi} \text{ (from FWR)}$$

$$= \frac{2 \times 0.12}{\pi} = \frac{0.14}{\pi} A$$

DC power drawn from battery is

$$P_{dc} = V_{CC} I_{dc}$$

$$= 15 \times \frac{0.14}{\pi} = 1.146W$$

AC power delivered to load is

$$P_{o(ac)} = \frac{1}{2} \frac{V_P^2}{R_L} = \frac{1}{2} \frac{(12)^2}{100}$$

$$= 0.72W$$

4 Power dissipated in both transistors is

$$1.146 - 0.72W = 0.426W$$

and power dissipated by each transistor

$$\text{is } \frac{0.426}{2} W = 0.213W = 213mW$$

Choice (B)

The cascade amplifier is a multistage configuration of

- A)CC-CB
- B)CE-CB
- C)CB-CC
- D)CE-CC

SOLUTION : B


cascade amplifier is a multistage configuration of CE-CB

6. A cascade connection of two voltage amplifiers A1 and A2 is shown in the figure. The open-loop gain A_{v0} , input resistance R_{in} , and output resistance R_o for A1 and A2 are as follows:

A1: $A_{v0} = 10$, $R_{in} = 10 \text{ k}\Omega$, $R_o = 1 \text{ k}\Omega$

A2: $A_{v0} = 5$, $R_{in} = 5 \text{ k}\Omega$, $R_o = 200 \Omega$

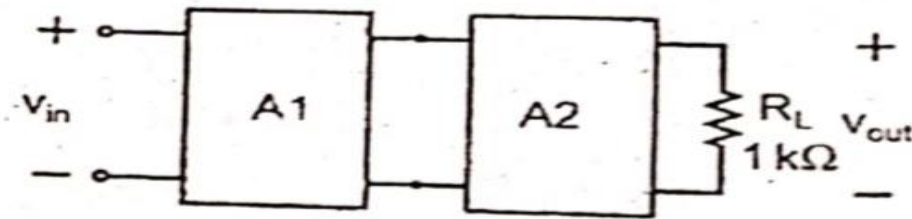
The approximate overall voltage gain V_{out}/V_{in} is _____.



(GATE 2014, Set-2)

$$6. \quad A_{V_{L1}} = A_V \frac{Z_{i2}}{Z_o + Z_{i2}}$$
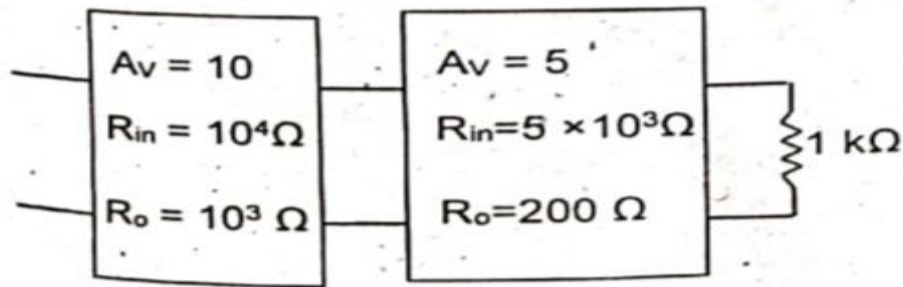
$$= 10 \left[\frac{5 \times 10^3}{10^3 + 5 \times 10^3} \right] = \frac{50}{6}$$



$$A_{V_{L2}} = 5 \left[\frac{1 \times 10^3}{200 + 10^3} \right] = \frac{5}{1.2}$$

$$A_{V_T} = A_{V_{L1}} \cdot A_{V_{L2}} = \frac{50}{6} \times \frac{5}{1.2} = 34.7$$

Ans: 34 to 35.3

Thank you